
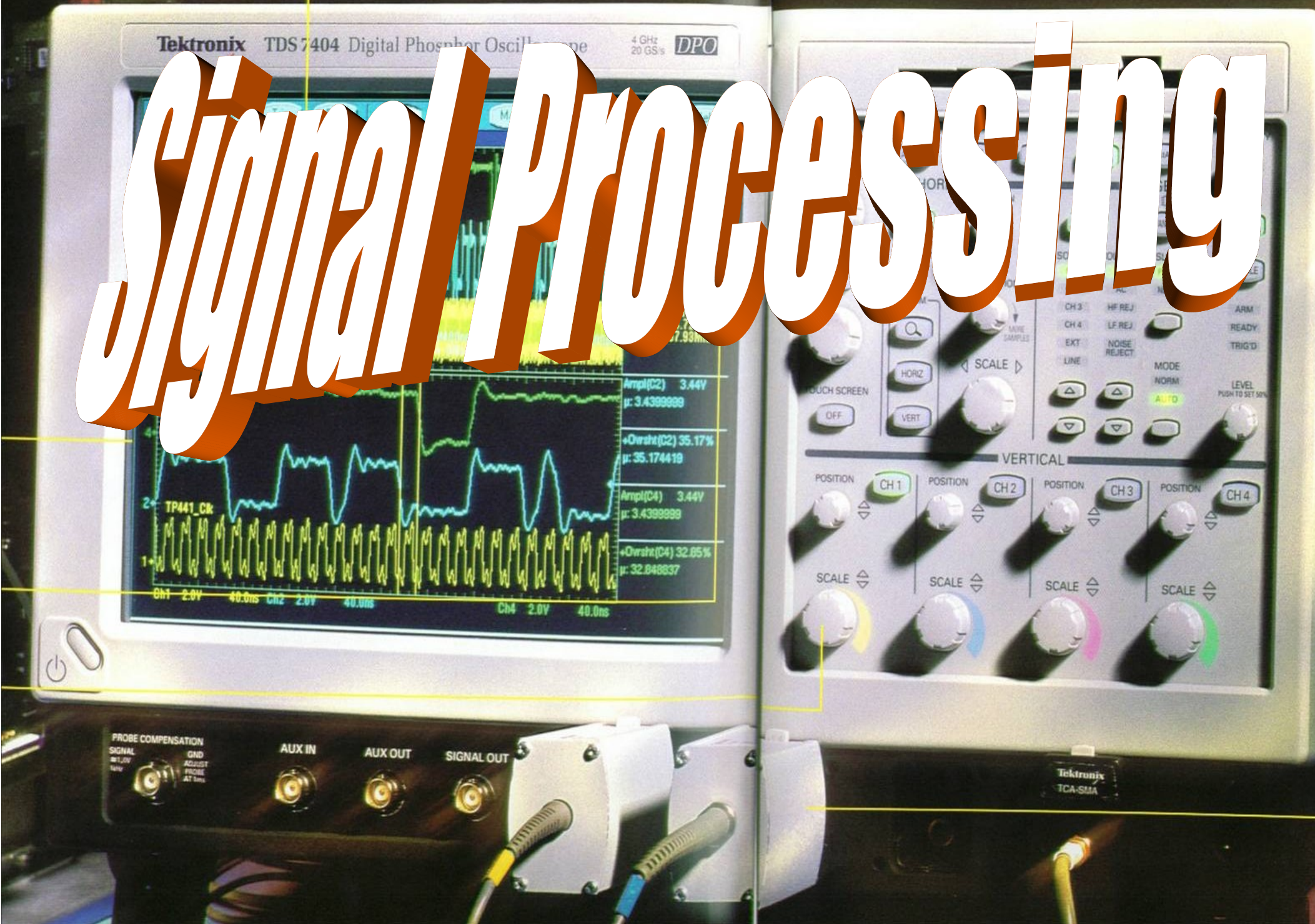


Signal Processing

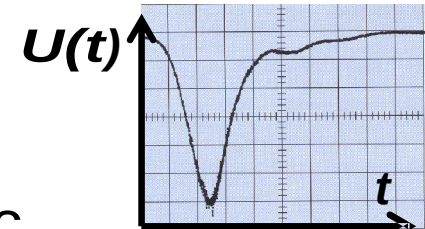


PM Operation



Fast PM: pulse rise time $\sim 2\text{ns}$, gain: $3 \cdot 10^7$



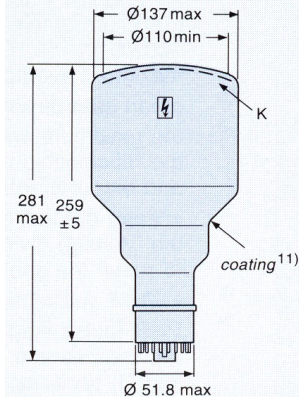
Philips XP2041
5" dia cathode
14 dynodes
+ focussing
electrodes




Socket FE1120
pin connections

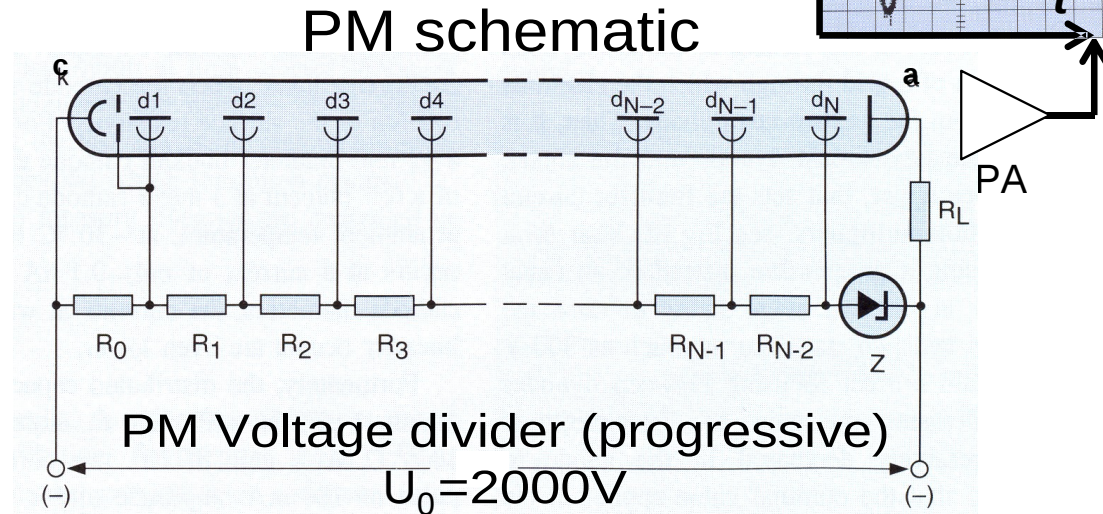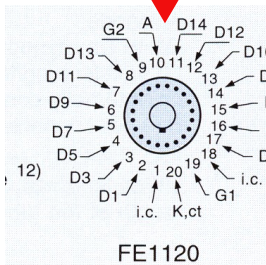

Sockets

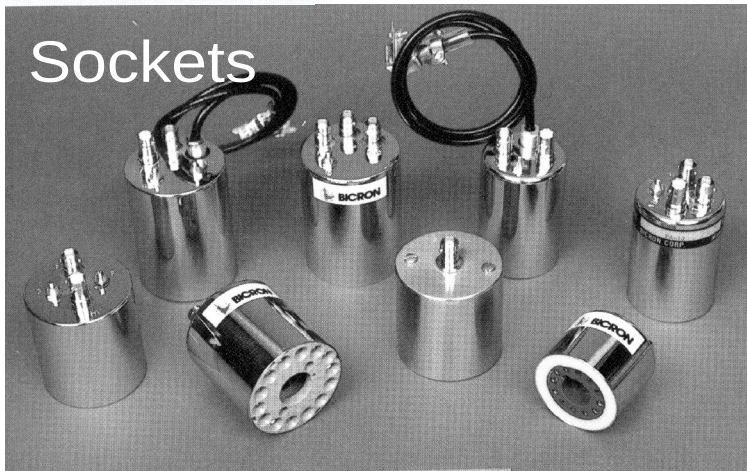

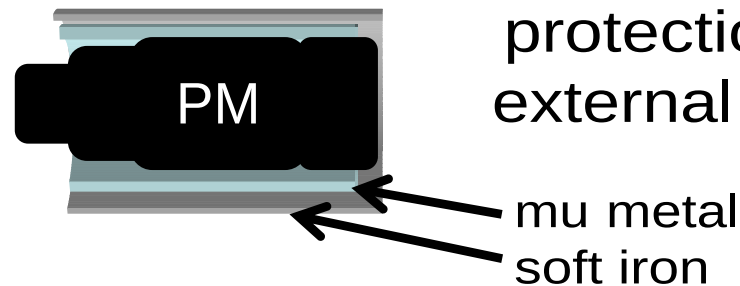mu-metal shield
tube provides
protection from
external B field.



Pre-Amplifiers

Task: amplify weak detector signals (mV) to $\sim 1\text{V}$, transmit through cable.
Main types: charge-sensitive or voltage-sensitive

Charge sensitive preamps integrate charge $Q(t) \propto E_{\text{deposit}}$ from detector directly. Use for semiconductor diodes.


Voltage sensitive preamps amplify $U(t) = Q(t)/C$, $C = \text{const.}! \rightarrow \text{PM, PC}$

Detector is essentially a capacitor C_d , delivers a time dependent charge $Q(t)$, current $I = dQ/dt$


For E measurement, integrate Q

For t measurement, differentiate Q

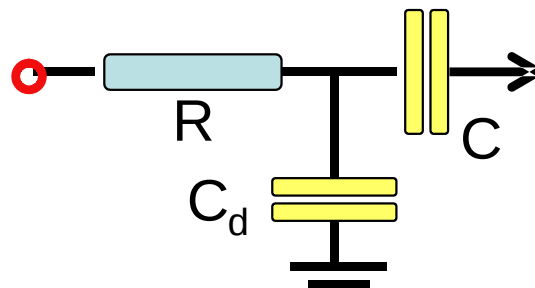Use operational amplifiers (*op-amp*) for both.




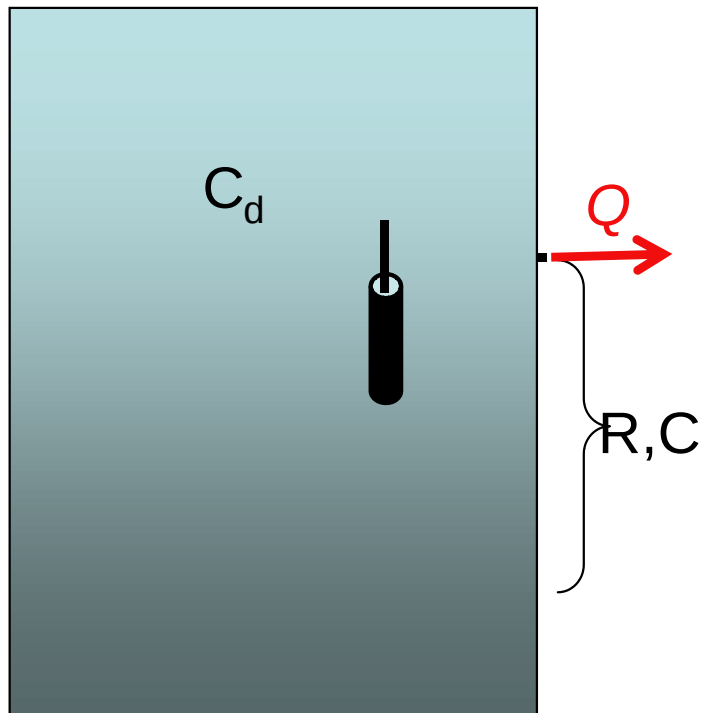Replacement circuit for detector and decoupling



Basic Counting System

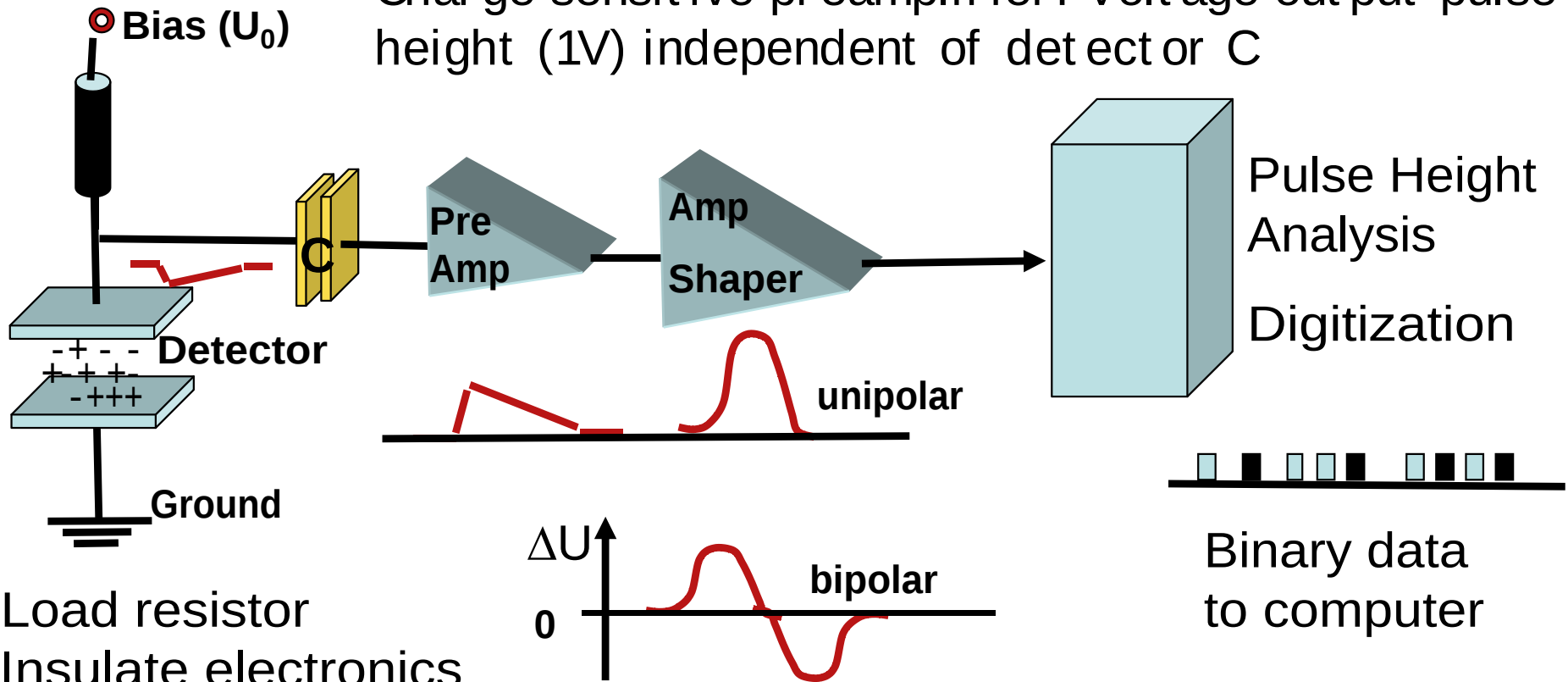Charge sensitive preamplifier: Voltage output pulse height (1V) independent of detector or C




R: Load resistor
C: Insulate electronics from high voltage (bias)
Pulse height 100 mV

Amplifier/Shaper:
differentiates (1x or 2x)


Final amplitude 2-10V

Operational Amplifiers

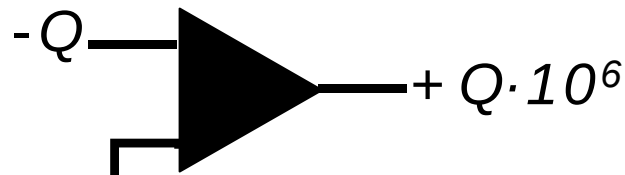


Gain is very high ($\sim 10^6$), inverting.
Properties of amp can be determined by feedback circuit:

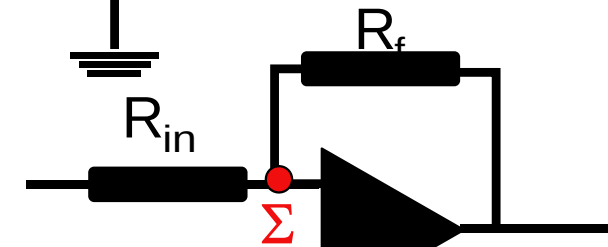Feeding back the negative of the input signal to the summation point cancels the signal at Σ



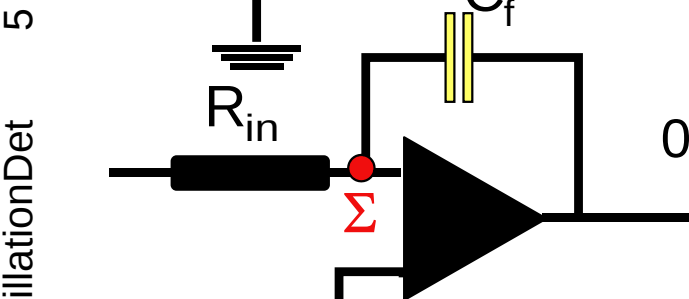
$$I_{\Sigma} = 0 = I_{in} + I_f = \frac{U_{in}}{R_{in}} + \frac{U_{out}}{R_f} \rightarrow U_{out} = -\frac{R_f}{R_{in}} \cdot U_{in}$$



$$0 = I_{in} + I_f = \frac{U_{in}}{R_{in}} + C_f \frac{dU_{out}}{dt} \rightarrow U_{out} = -\frac{1}{R_{in}C_f} \cdot \int U_{in} dt$$


Integrator

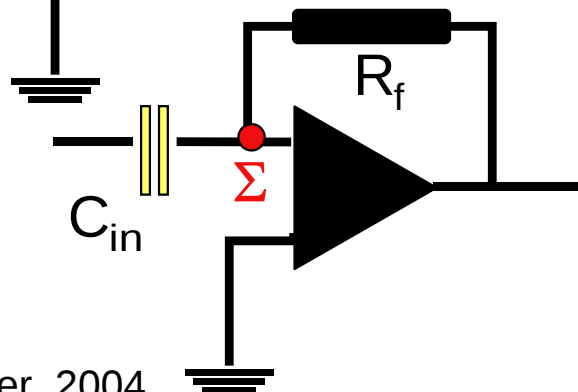

$$U_{out} = -C_{in}R_f \frac{dU_{in}}{dt}$$

Differentiator


Charge Sensitive Preamplifier

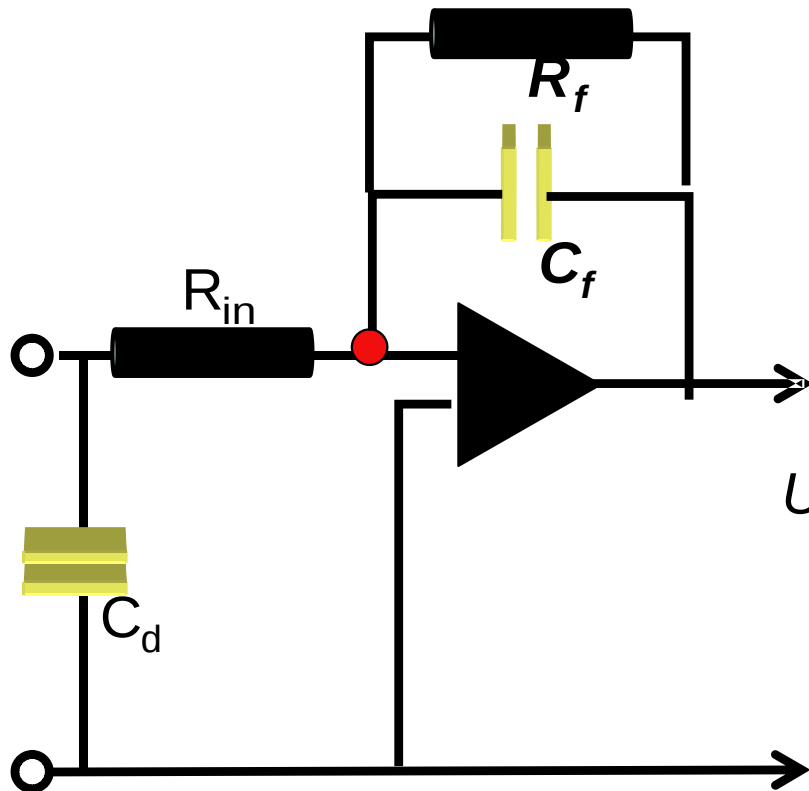

Inverting, integrating preamp


Pulse decay governed by
 $t_{dec} \approx 1/R_f C_f$.

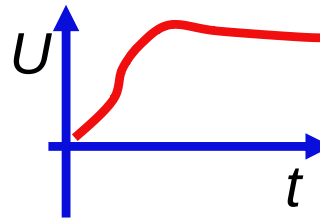Additional amplifier necessary
for pulse shaping and gain.



Main/ Shaping Amplifiers


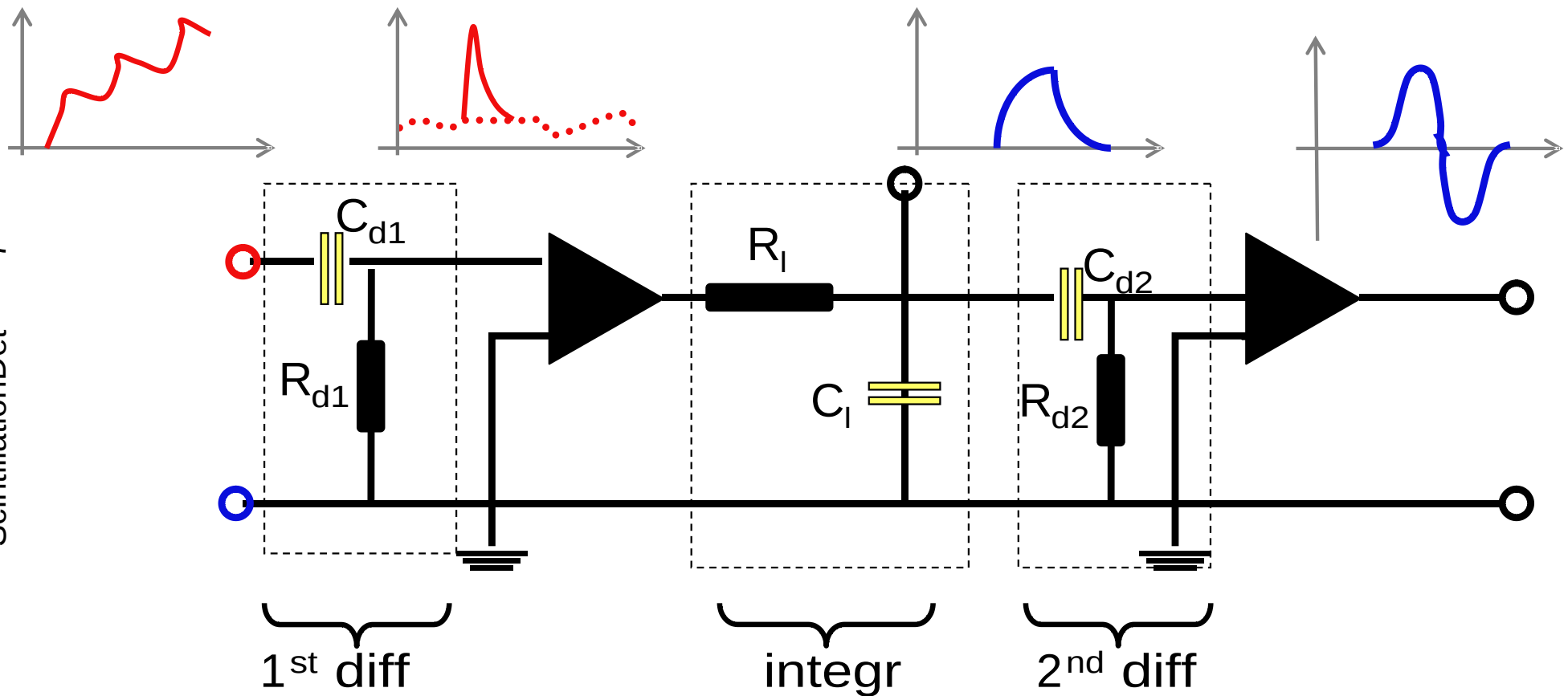
- Tasks:
- 1) **Linear** amplification to pulse heights of $U \approx (1-10)V$
 - 2) Improvement of signal/noise ratio (integration)
 - 3) Pulse shaping (Gaussian shape is best)



More versatility: RC-circuits $\rightarrow$ active filters

NIM Signal Standards

(National Instruments Methods)

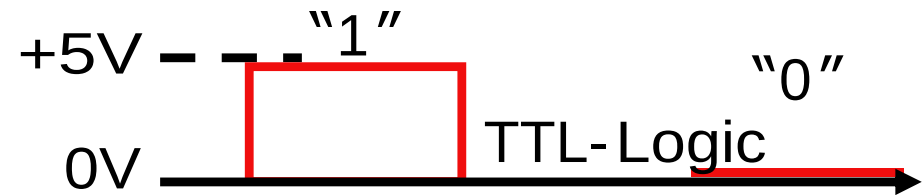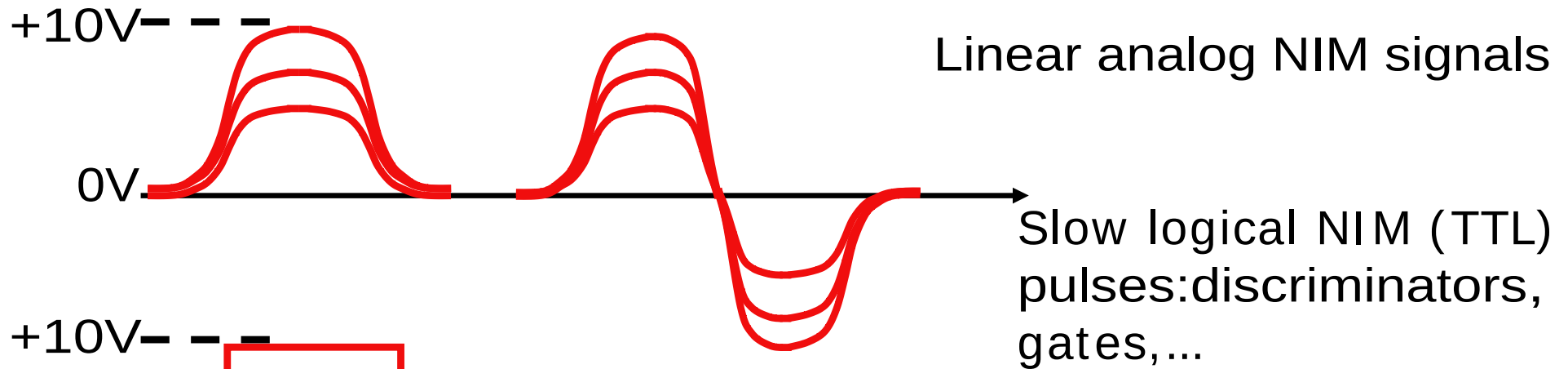


$\leq 2\text{ns}$

-16mA
-0.8V/50Ω


Fast logical NIM signals for fast timing/triggering

NIM-gate/trigger signal

Discriminator/Trigger

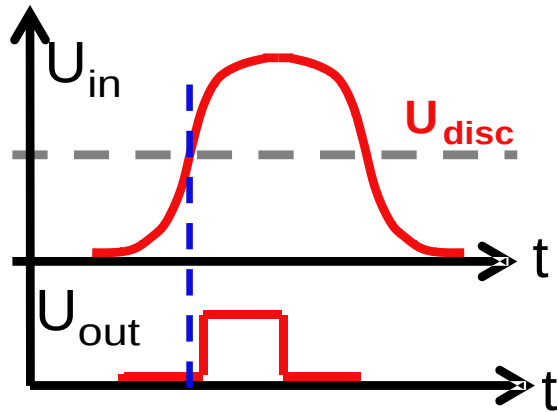


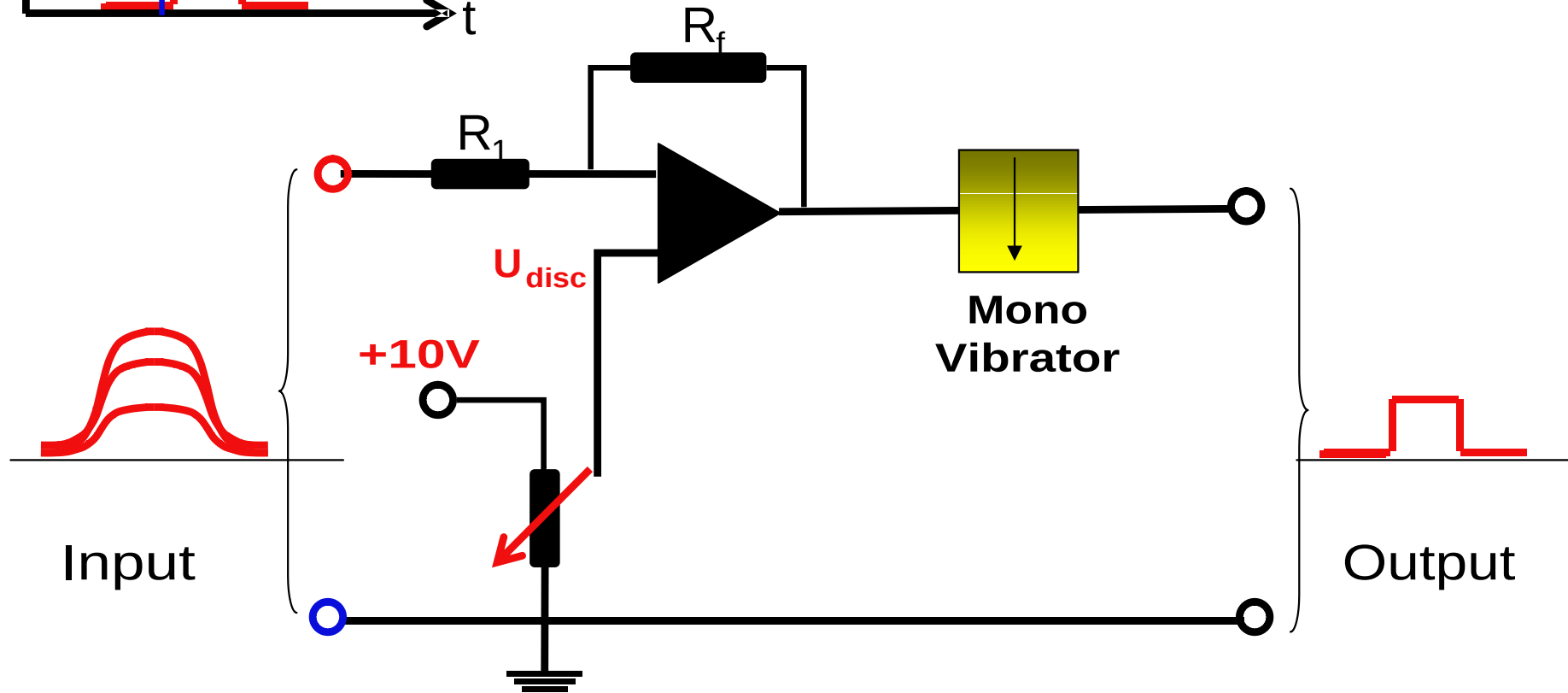Task: Produce a logical signal, whenever analog signal exceeds threshold U_{disc} . Use for logical decisions (open acquisition,...). Exist for slow and fast pulses.



For fast timing, use negative NIM logic units

Zero-Crossing Triggering

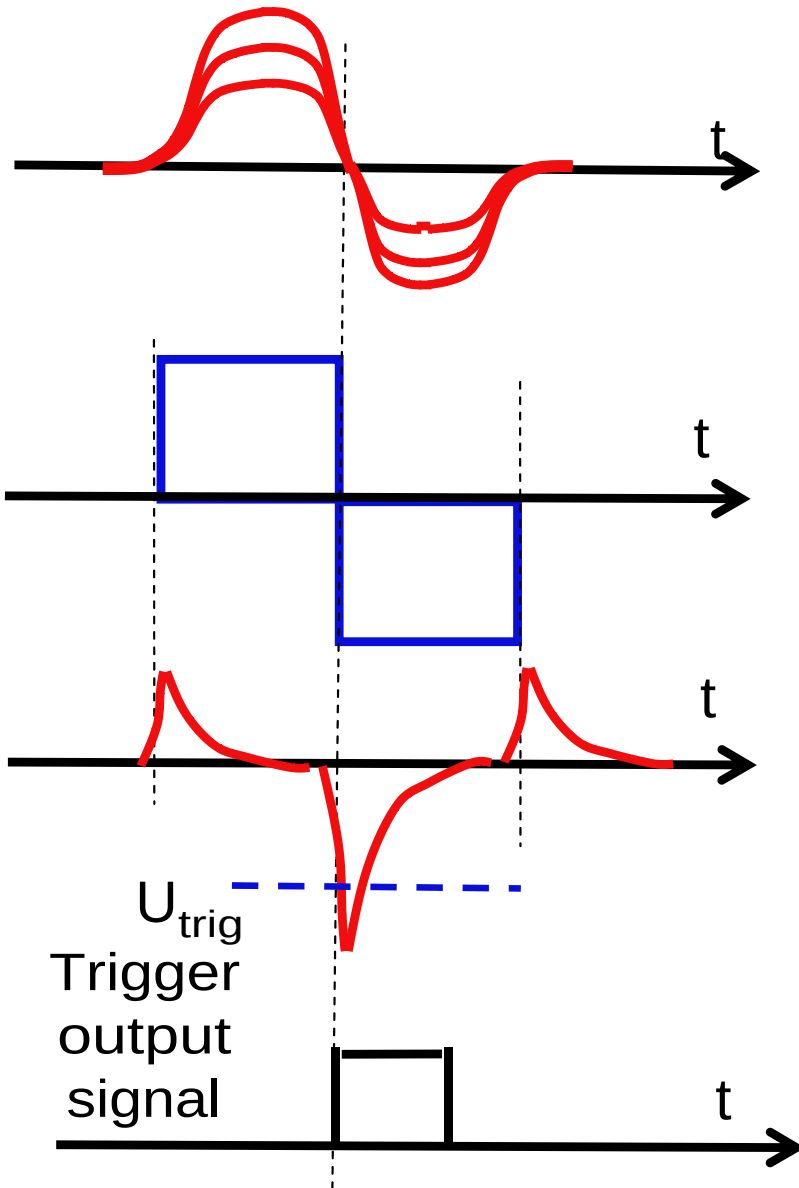

Produce fast, bipolar linear pulse. Possible: different gains for positive and negative parts $\rightarrow$ zero crossing at different time (fraction of time to maximum)


Produce "saturated" uniform pulse

Differentiate saturated pulse, use triplet pulse as input for trigger (negative pulse polarity).

Trigger output appears at zero crossing

(Internal delays neglected)


Constant-Fraction Discriminator

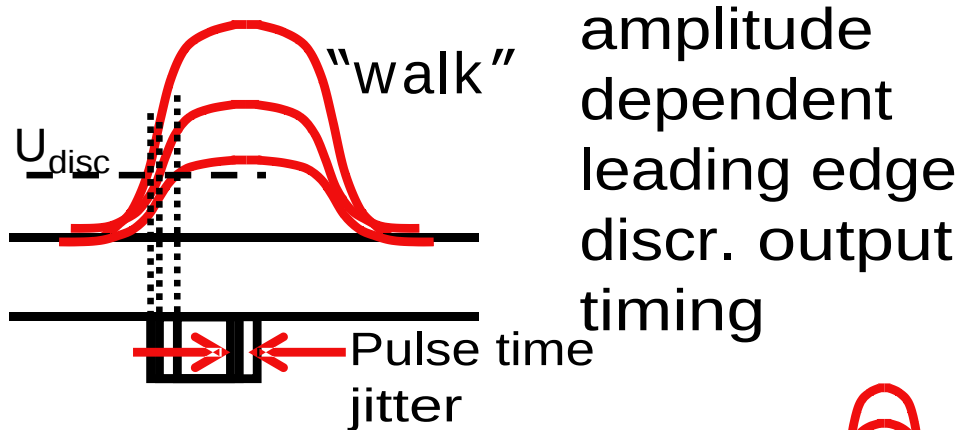

amplitude
dependent
leading edge
discr. output
timing

Zero crossing timing
always at same physical
time, independent of
pulse amplitude for fixed
pulse shape: no "walk"
with energy




11
ScintillationDet

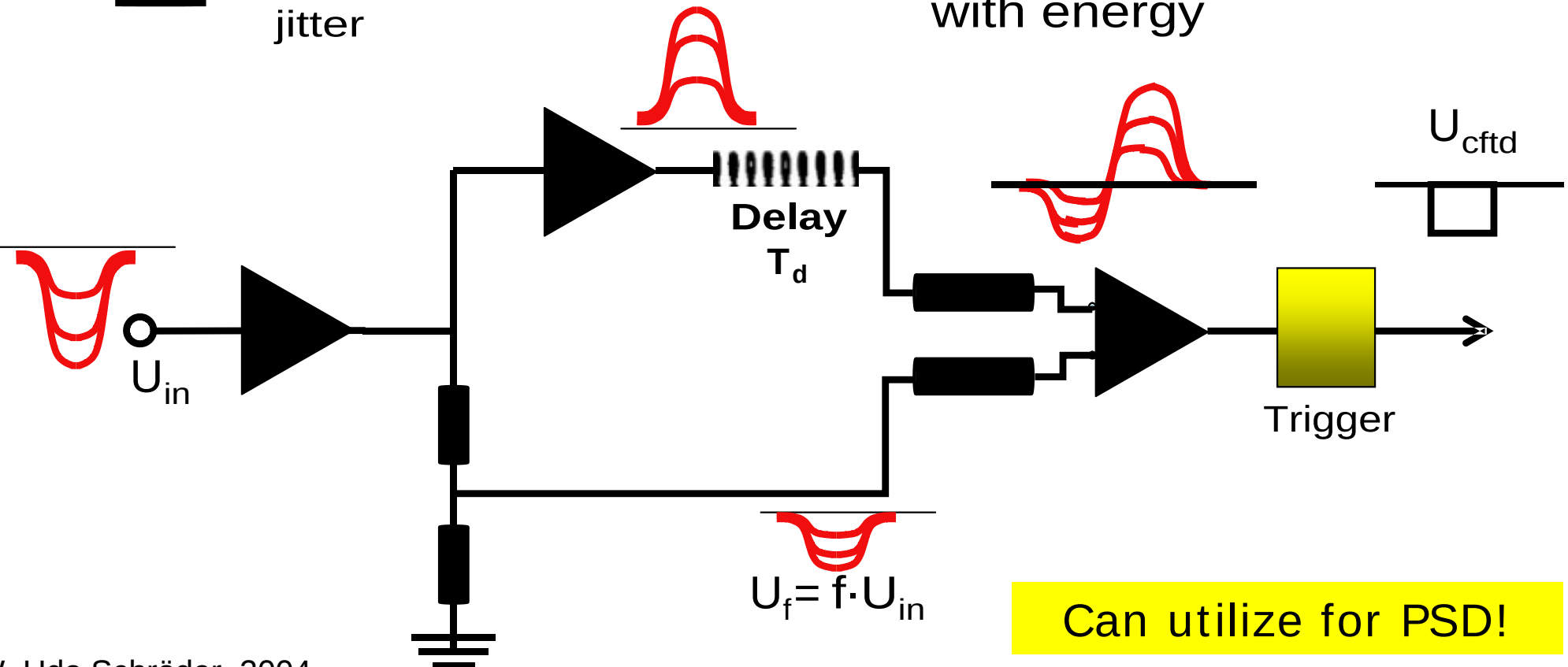



Can utilize for PSD!

Logic Modules


Overlap Coincidence

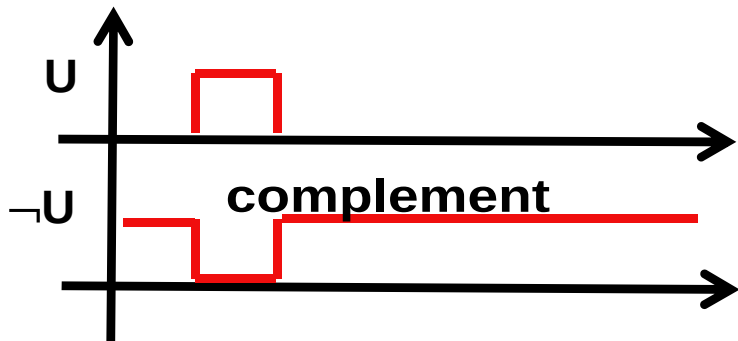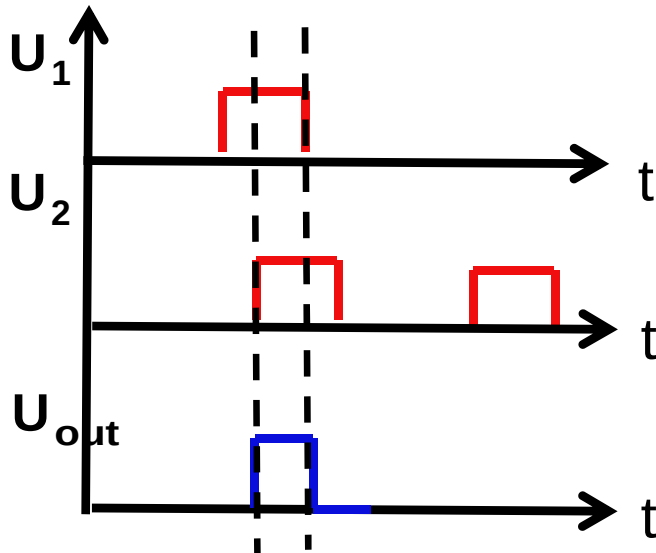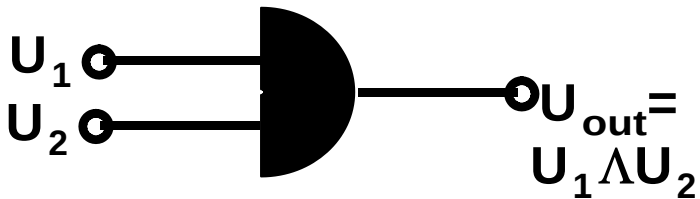

Or (inclusive)

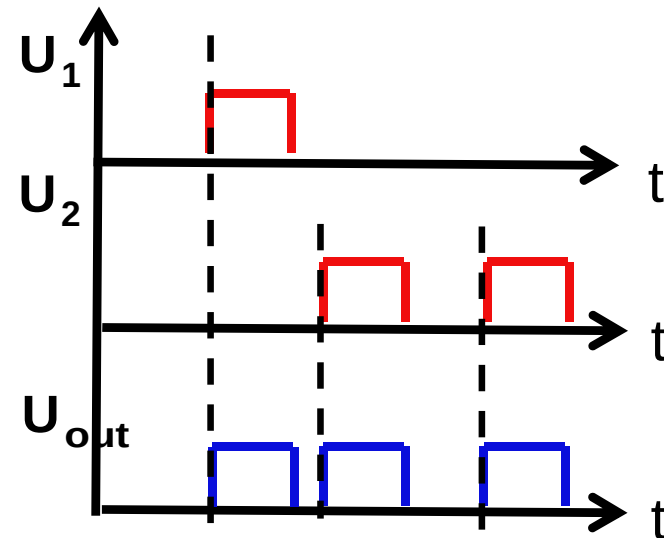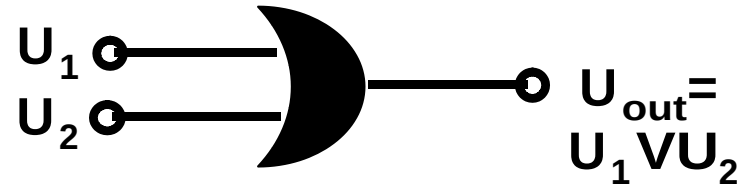


For fast timing:
use fast negative logic

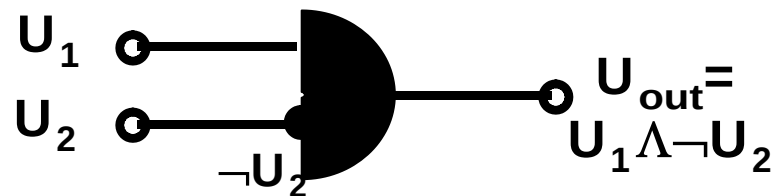

Anti-Coincidence

Signal Transmission

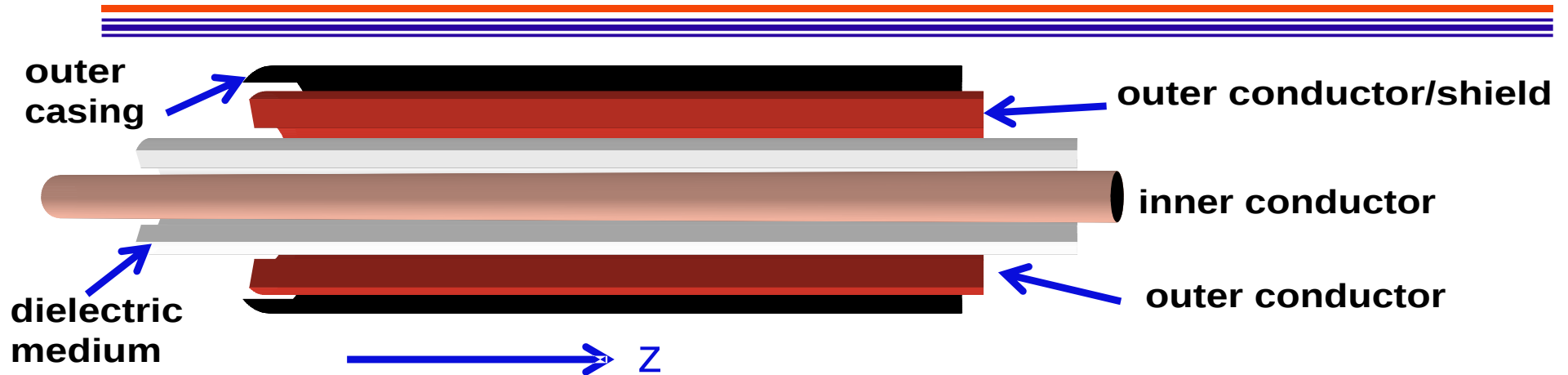

Coaxial cables/transmission lines $\leftrightarrow$ traveling waves in cavity resonators

Wave equation ($R=0$):

$$\frac{\partial^2 U}{\partial z^2} = L \cdot C \cdot \frac{\partial^2 U}{\partial t^2}$$

L : inductivity/length
 C : capacity/length
 depend on diameter
 and dielectric

signal propagation
 speed (speed of light):

$$c = 1/\sqrt{LC}$$

typically $c^{-1}=5$ ns/m


characteristic resistance
 Z_0 = Ohmic resistance!

$$Z_0 = \sqrt{L/C}$$

$Z_0 = 50 \Omega$ or 93Ω
 used for timing,
 spectroscopy, resp.

For $R \neq 0$, $Z_0(\omega)$ complex

Impedance Matching

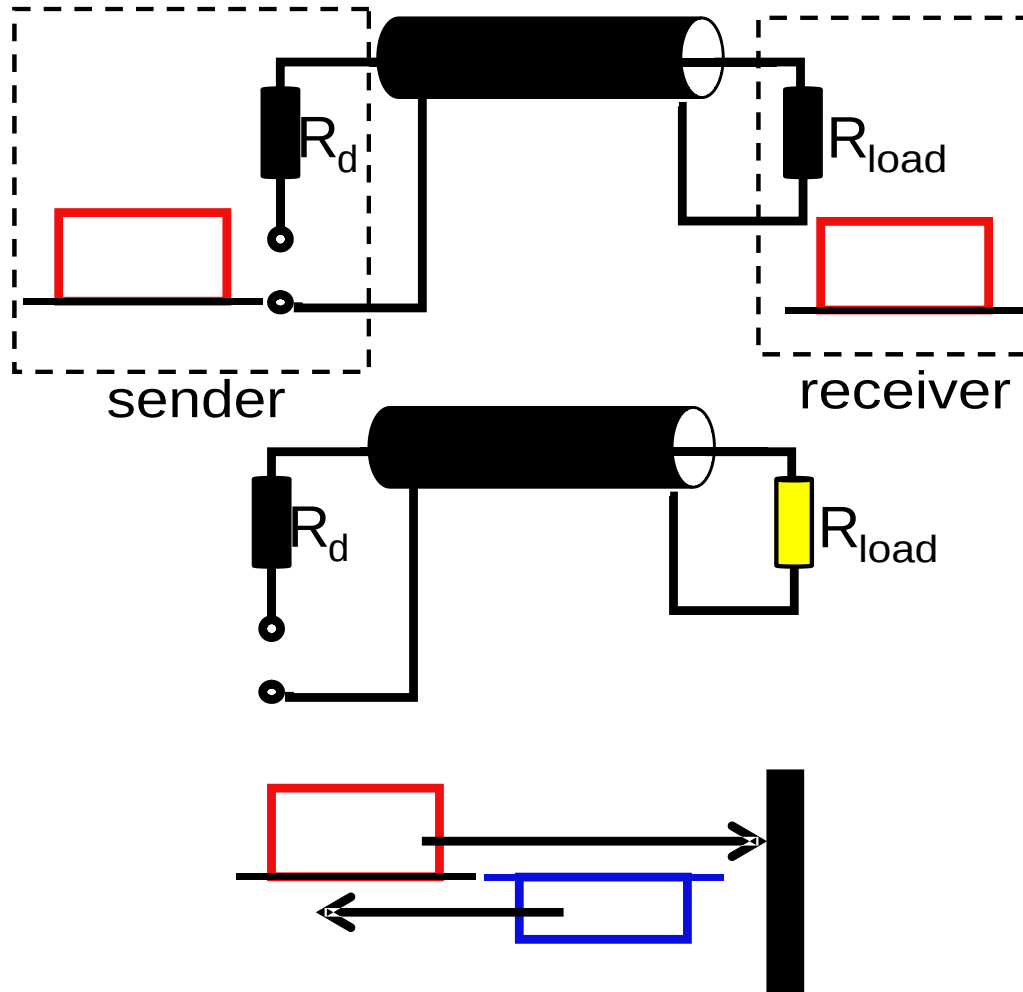


For impedance matching, $R_{load} = Z_0$, cable looks infinitely long: no reflections from end.

For mismatch, $R_{load} \neq Z_0$, reflection at end, traveling back, superimpose on signal


$$\frac{U_{refl}}{U_{in}} = \frac{R_{load} - Z_0}{R_{load} + Z_0}$$

Polarity of reflected signal $R_{load} = 0, \infty$

Cable Reflections

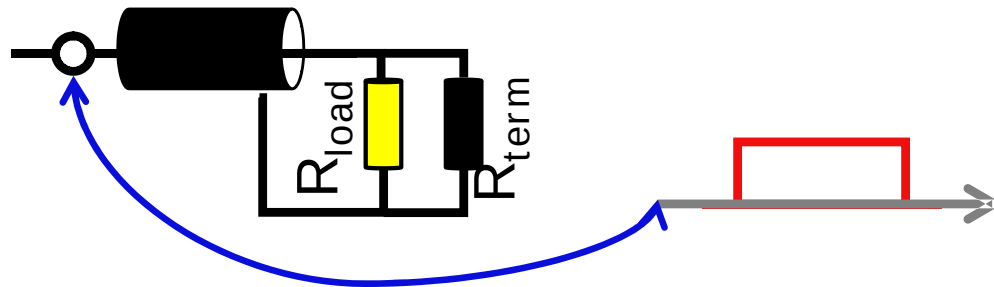


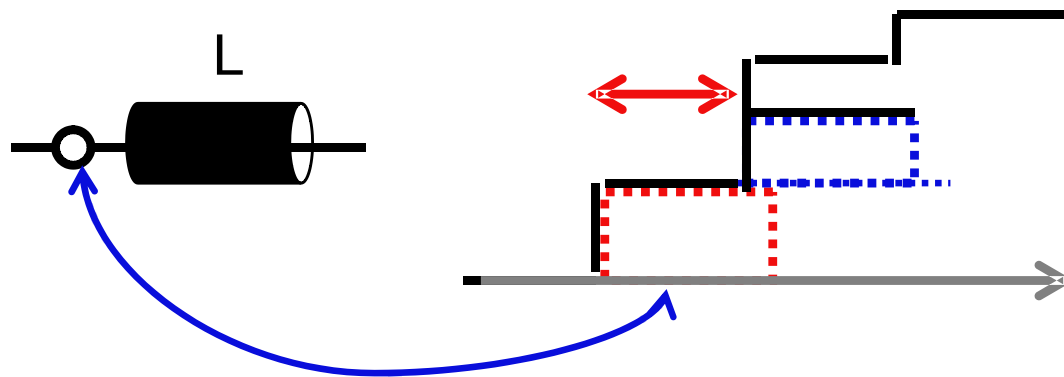Receiver input impedance $R_{load} \neq Z_0$,
 $\rightarrow$ use additional Ohmic termination in parallel



Open end: $R_{load} = \infty$
 Input and reflection equal polarity, overlap for $t > 2T_{cable}$

$$T_{cable} = 2L/c$$

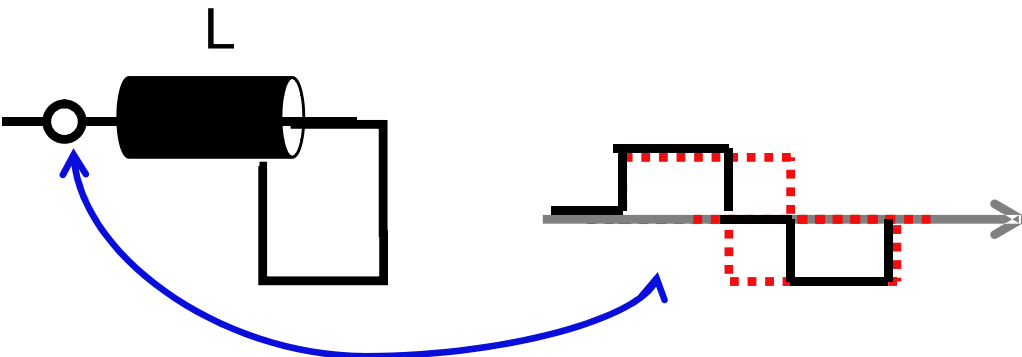

Short: $R_{load} = 0$, Input and reflection opposite polarity, superposition = bipolar

Multiple (n) reflections attenuated by R^{-n}



The End

This document was created with Win2PDF available at <http://www.daneprairie.com>.
The unregistered version of Win2PDF is for evaluation or non-commercial use only.